

The background is a dark navy blue. It features several horizontal, wavy bands of white and gold lines. Interspersed among these bands are solid-colored rectangular blocks in blue and gold. Some of these blocks have small black dots. The text 'EE221' is written in red on a gold block.

EE221

Transformers

Tutorial


🕒	✓	<u>OBJECTIVES</u>
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Basic use of transformer (T/F)
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Types and Construction
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Ideal T/F
	<input type="checkbox"/>	
•	<input type="checkbox"/>	voltage and current ratio
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Dot Convention
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Equivalent Circuit of T/F
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Determining components values
	<input type="checkbox"/>	
•	<input type="checkbox"/>	PV system
	<input type="checkbox"/>	
•	<input type="checkbox"/>	Voltage Regulation
	<input type="checkbox"/>	

[illegible]

Transformers

A transformer is a device that changes ac electric power at one frequency and voltage level to ac electric power at the same frequency and another voltage level through the action of a magnetic field.

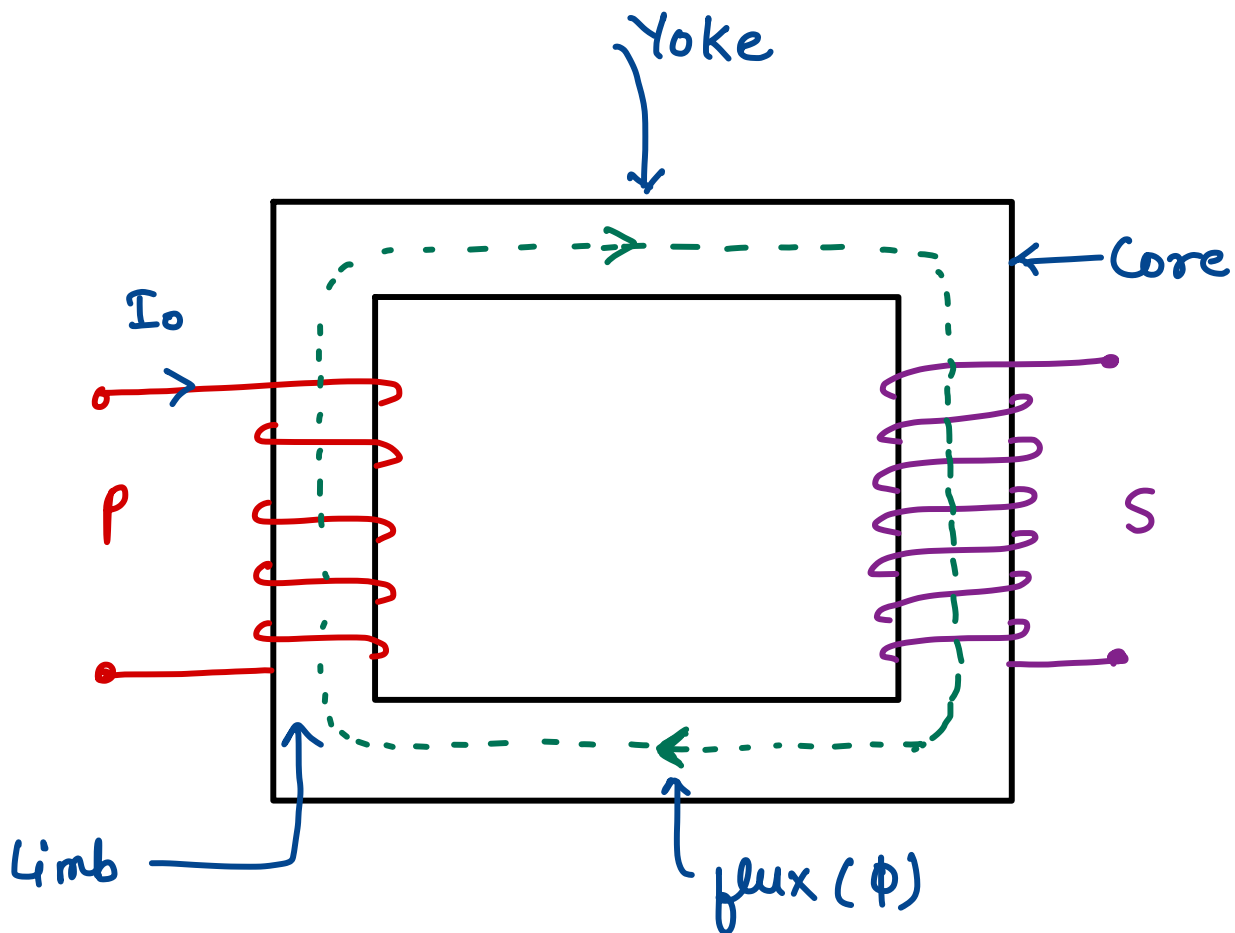It consists of two or more coils of wire wrapped around a common ferromagnetic core. These coils are (usually) not directly connected. The only connection between the coils is the common magnetic flux present within the core.



Applications

- used to step-up generator voltage to an appropriate voltage level for power transfer.
- stepping down the transmission voltage at various levels for distribution and power utilization.

Why T/F are used ??

In a modern power system, electric power is generated at voltages of 12 to 25 kV. Transformers step up the voltage to between 110 kV and nearly 1000 kV for transmission over long distances at very low losses. Transformers then step down the voltage to the 12- to 34.5-kV range for local distribution and finally permit the power to be used safely in homes, offices, and factories at voltages as low as 120 V.

$$P = VI$$

if V generated = low

& P demand = high

$\therefore I \rightarrow$ high

$$\textcircled{*} \text{ losses} = I^2 R$$

$I \text{ high} \Rightarrow \text{losses high}$

$$\textcircled{*} V \text{ drop} = IR$$

$I \text{ high} \Rightarrow V \text{ drop high}$

Transformer classifications

1. Number of windings

- Conventional T/F : two windings
- Auto-T/F : one winding
- others : more than two windgs.

2. Number of phases:

- Single-phase T/F
- Three-phase T/F

T/F classifications contd...


3. Voltage level at which wndg is operated:

- step-up T/F : primary wndg is a low voltage (LV) wndg.
- step-down T/F : primary wndg is a high voltage (HV) wndg.


4. Construction:

- Core type T/F
- Shell type T/F

Constructional Details

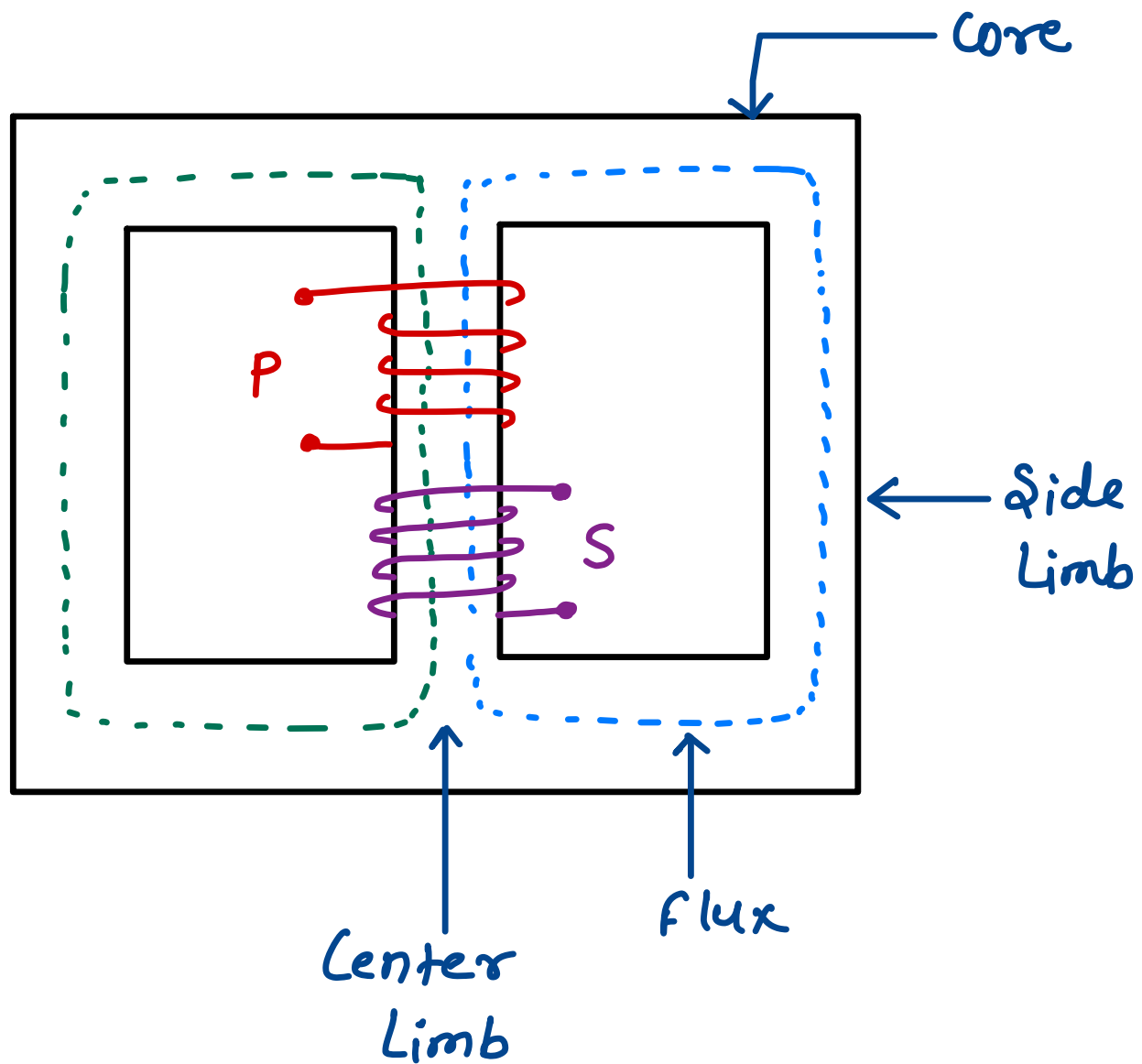

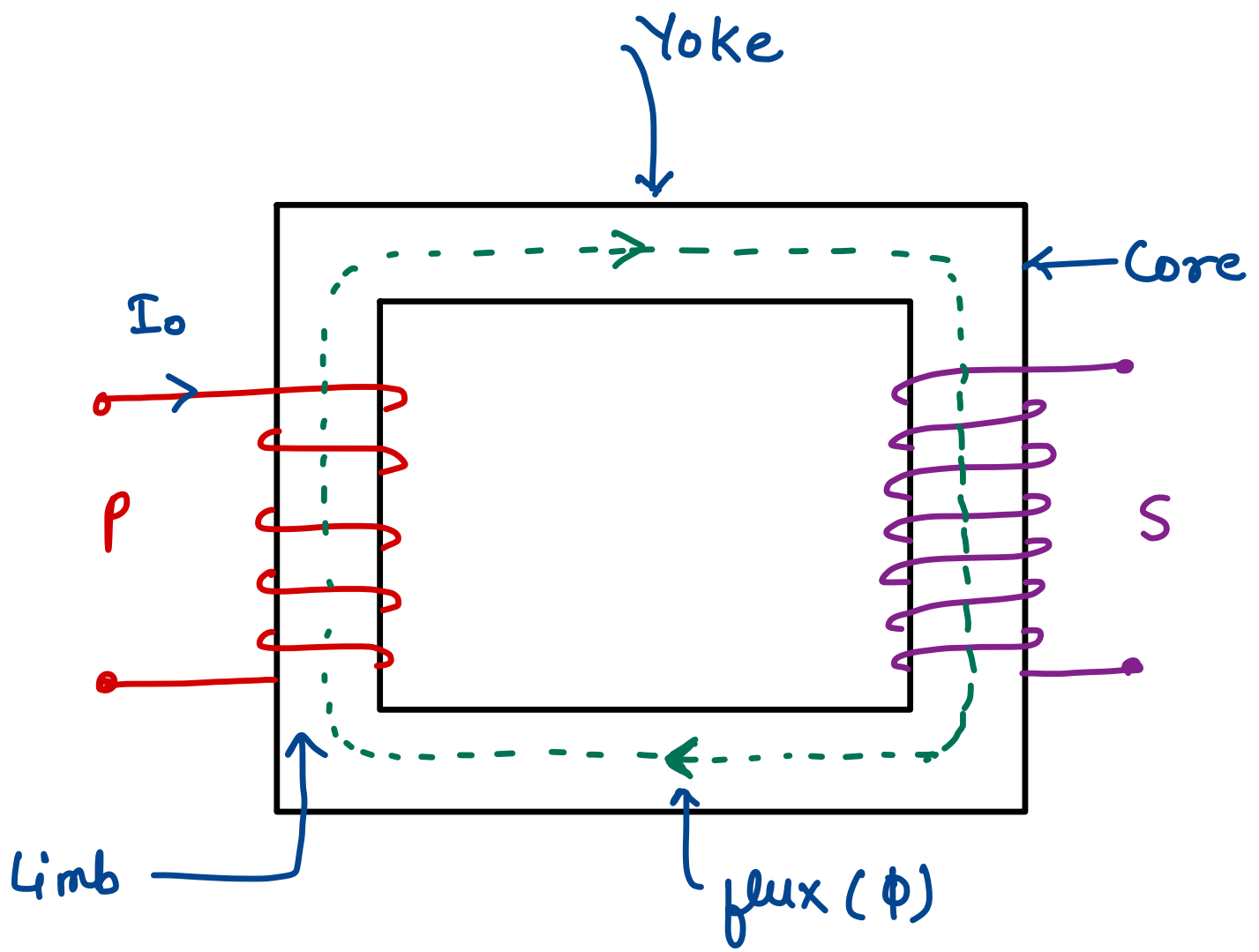Shell Type TIF : windgs are wrapped around the center leg of a laminated core.




Core Type T/F :

wndgs are wrapped around two sides of a laminated square core.

Primary & Secondary Windings

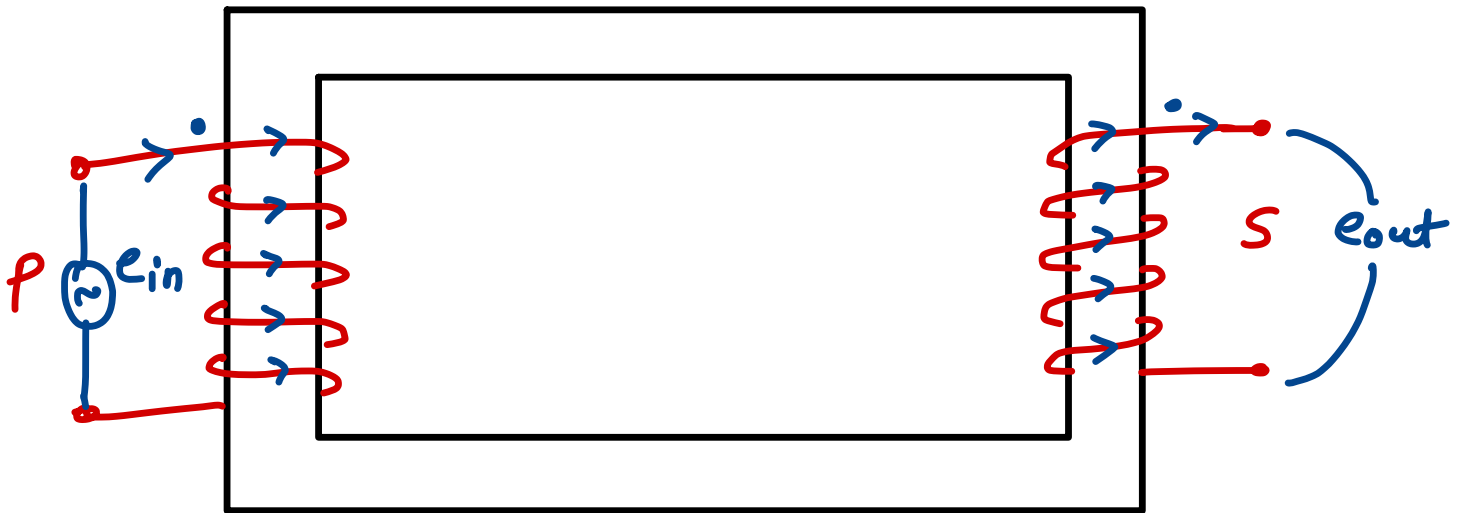A two-winding TIF consists of two windings interlinked by a mutual magnetic field.



Primary wdg: energized by connecting it to an input source.

Secondary wdg: wdg to which an electrical load is connected and from which output energy is drawn.


Fundamentals :

1. A voltage is induced in a coil when it links a variable flux.
2. A sinusoidal flux induces a sinusoidal voltage.

Ideal T/F :

↳ is a lossless device with an input winding and an output winding having following properties :

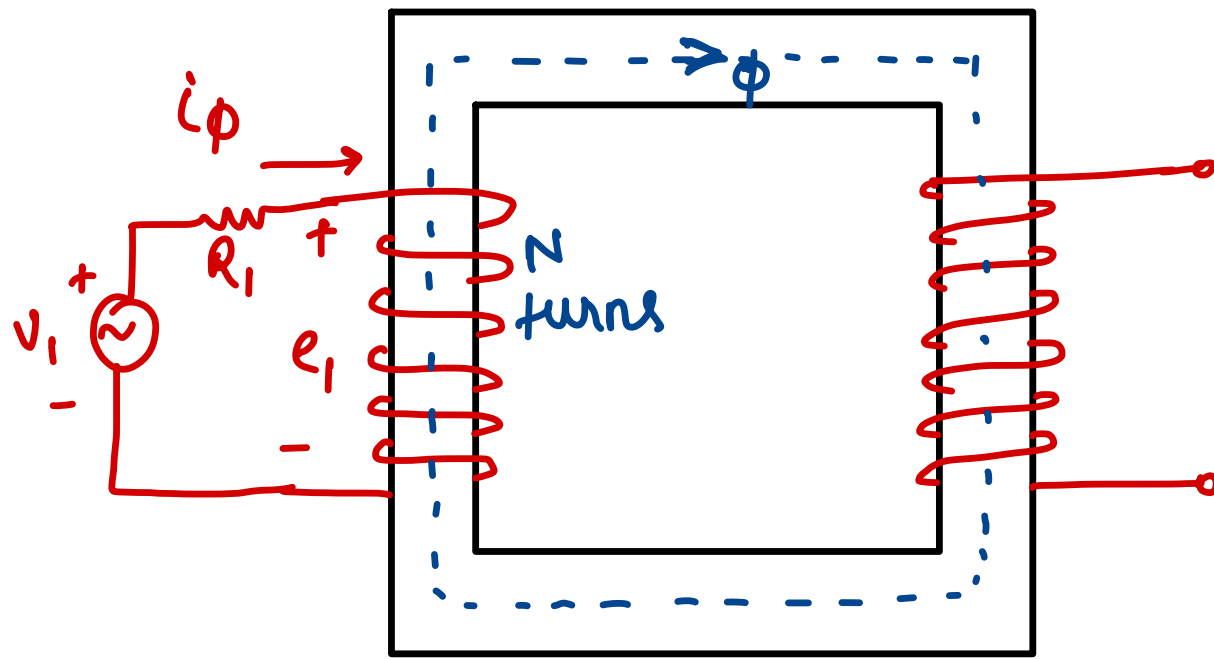- No iron and copper losses.
- No leakage fluxes.
- A core of infinite magnetic permeability and of infinite electrical resistivity
- Flux is confined to the core and wdg resistances are negligible.



- AC current i_ϕ flows through primary winding.

\Rightarrow establishes an alternating flux in mag. ckt.

\Rightarrow flux induces an emf in primary

$$e_1 = \frac{d\lambda_1}{dt} = \frac{d(N_1\phi)}{dt} = N_1 \frac{d\phi}{dt}$$

where,

λ_1 = flux linkage of primary wdg

Φ = flux in the core linking both
windgs [wb]

N_1 = no. of turns in primary
wdg.

e_1 \rightarrow induced emf [V]

$$V_1 = \underbrace{R_1 I_0}_{\text{no load resistance drop} \rightarrow 0} + e_1 \quad \text{--- (2)}$$

$$\Rightarrow \boxed{V_1 \simeq e_1}$$

Let $\phi = \phi_{\max} \sin \omega t$

then,

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$e_1 = \omega N_1 \phi_{\max} \cos \omega t$$

$$\therefore \omega = 2\pi f$$

$$e_1 = 2\pi f N_1 \phi_{\max} \cos \omega t$$

NOTE:

$$\phi = \phi_{\max} \sin \omega t$$

$$e_1 = 2\pi f N_1 \phi_{\max} \cos \omega t$$

\Rightarrow induced emf leads the flux by 90° .

RMS (Effective) value of e_1 :

$$\therefore e_1 = 2\pi f N_1 \Phi_{\max} \cos \omega t$$

\downarrow RMS $\rightarrow e_{\max}$



$$E_1 = \frac{e_{\max}}{\sqrt{2}}$$

$$\left[\because \text{RMS} = \frac{\text{peak}}{\sqrt{2}} \right]$$

$$\Rightarrow E_1 = \frac{2\pi f N_1 \Phi_{\max}}{\sqrt{2}}$$

$$\Rightarrow \boxed{E_1 = 4.44 f N_1 \Phi_{\max}}$$

Ideal T/F phasor diag.:

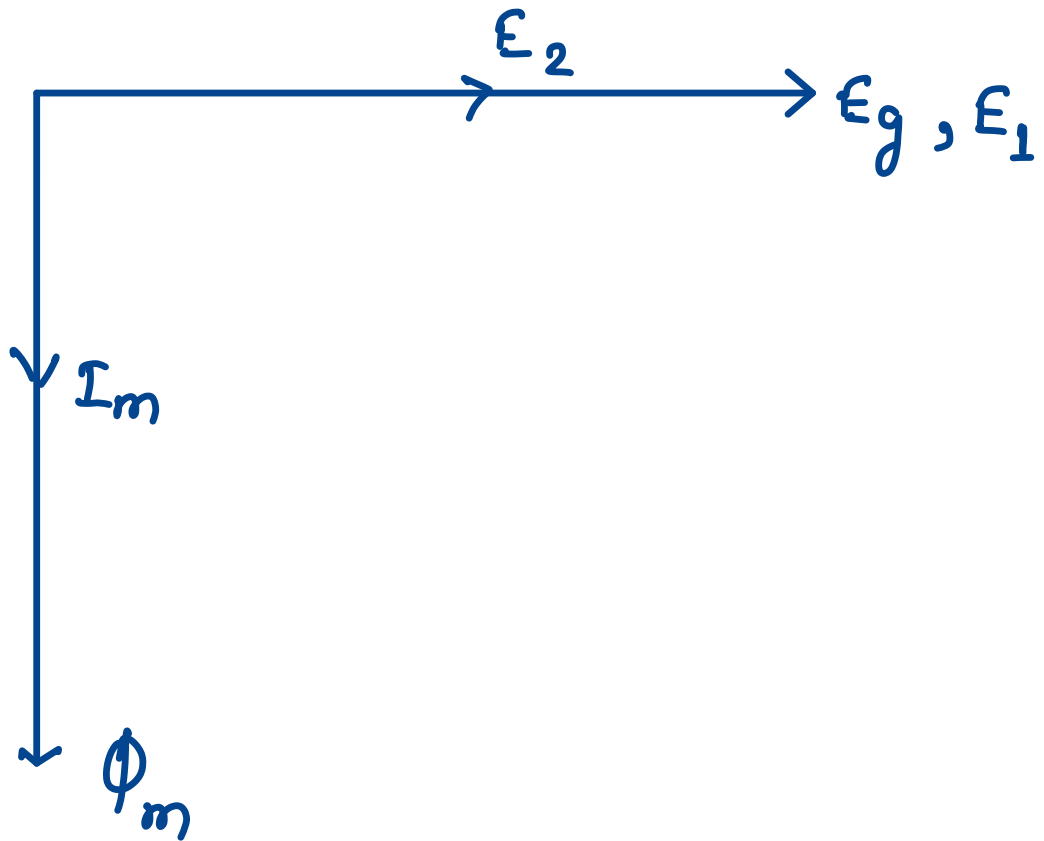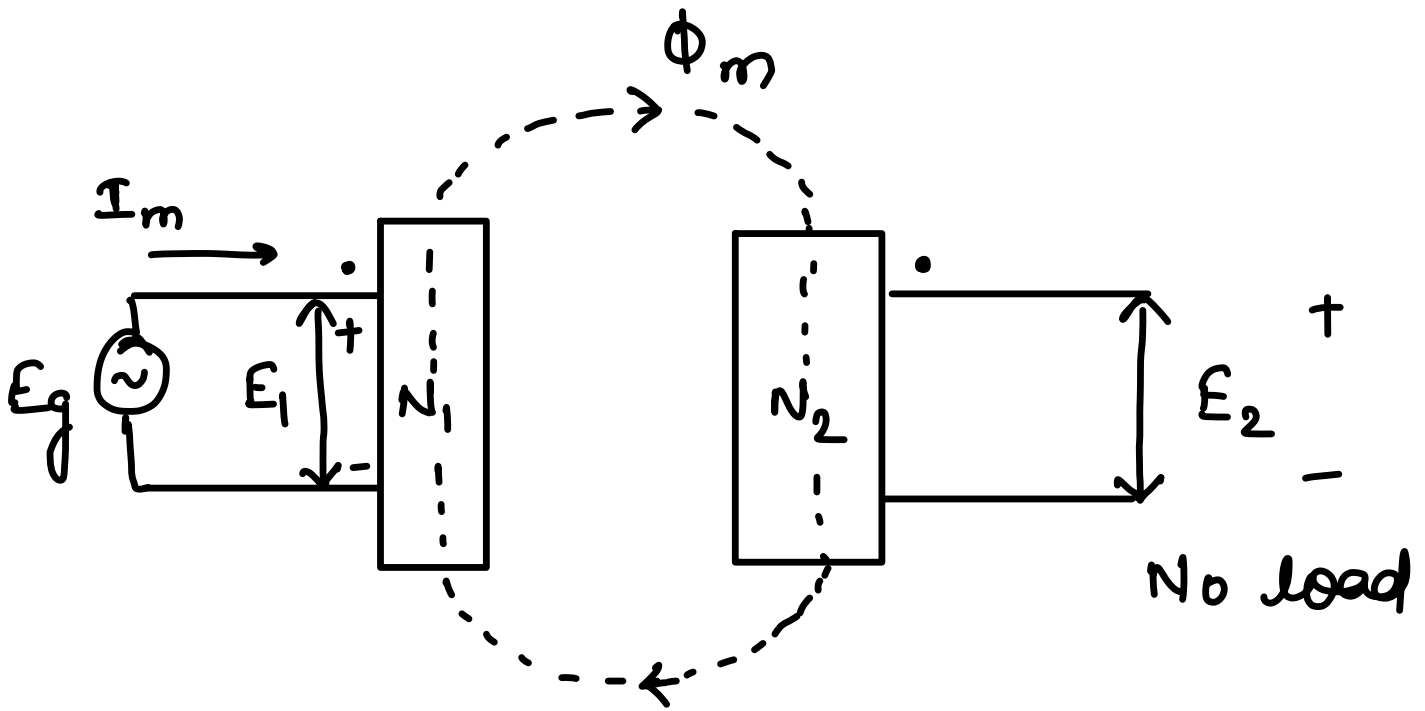

Formula:

$$E = 4.44 f N \Phi_{\max}$$

where,

E = effective voltage induced [V]

f = frequency of flux [Hz]

N = No. of turns on the
coil

Φ_{\max} = peak value of the
flux [wb]

Examples

1. The coil possesses 4000 turns and links an ac flux having a peak value of 2 mwb. If the frequency is 50 Hz, calculate the effective value and frequency of the induced voltage E .

Soln.

$$E = 4.44 f N \Phi_{\max}$$

$$= 4.44 \times 50 \times 4000 \times 0.002$$

$$= 1776 \text{ V}$$

$$\Rightarrow f = 50 \text{ Hz}$$

RMS
value

Voltage Ratio:

(Turns Ratio)

$N_1 \rightarrow$ primary
wndg turns

$N_2 \rightarrow$ Secondary
wndg turns



$E_g \rightarrow$ sinusoidal source

$I_m \rightarrow$ magnetizing current

$\Phi_m \rightarrow$ flux created by I_m
links both primary & secondary wndgs
mutual flux

$$E_1 = 4.44 f N_1 \Phi_{max} \quad \text{--- ②}$$
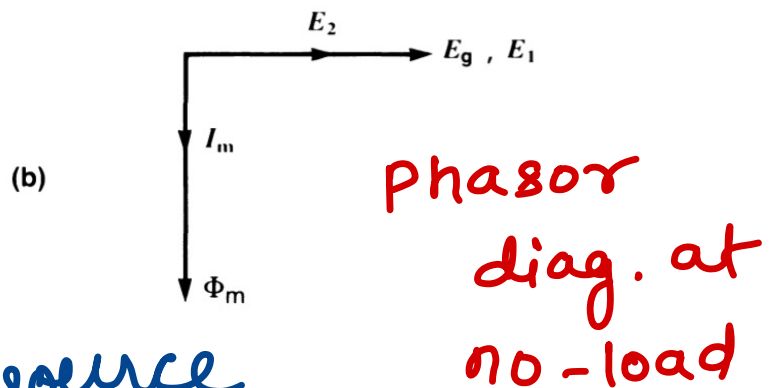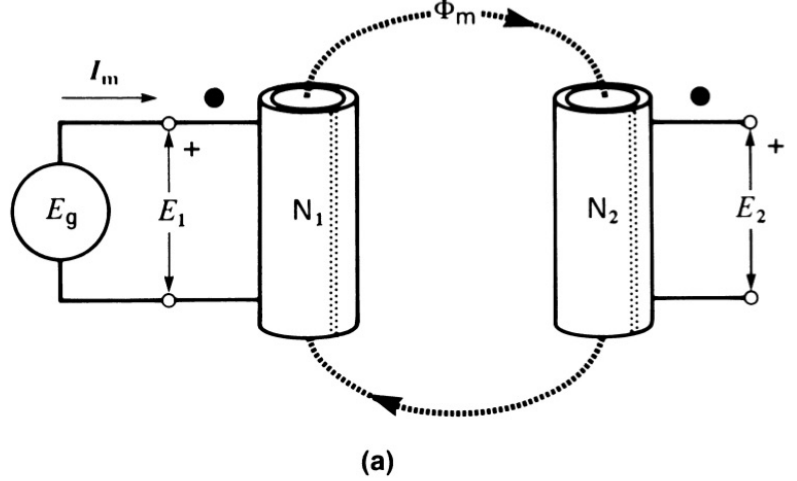
$$E_2 = 4.44 f N_2 \Phi_{max} \quad \text{--- ③}$$



∴ voltage ratio and turns ratio
are given as:

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = a$$

where,

$E_1 \rightarrow$ Emf induced in primary [V]

$E_2 \rightarrow$ " " " secondary [V]

$a \rightarrow$ turns ratio

Q. An ideal T/F having 90 turns on the primary and 2250 turns on the secondary is connected to a 120V, 50Hz source. The coupling between primary and secondary is perfect, but the magnetizing current is 4A.

Calculate:

a) Effective voltage across the secondary terminals.

$$\rightarrow E_1 = 120V$$

$$N_1 = 90$$

$$N_2 = 2250$$

$$\therefore \frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\Rightarrow E_2 = \frac{N_2}{N_1} \times E_1$$

$$= \frac{2250}{90} \times 120$$

$$E_2 = 3000 \text{ V}$$

(b) peak voltage across secondary terminals

$$\rightarrow \therefore \text{Effective value} = \frac{\text{peak}}{\sqrt{2}}$$

$$\Rightarrow \text{peak voltage} = \sqrt{2} \times E_2$$

$$= \sqrt{2} \times 3000$$

$$E_{2\text{peak}} = 4242 \text{ V}$$

(c) Instantaneous voltage across the secondary when the instantaneous voltage across the primary is 37V.

$$\therefore \frac{E_2}{E_1} = 25$$

$$\therefore e_1 = 25 e_2$$

$$= 25 \times 37$$

$$e_1 = 925 \text{ V}$$